

First Name:

Last Name: Answer

School of Computer Science
CS 2614: Computer Organization
Spring 2025
Quiz 4

Q. 1 Using a decoder and external gates, design the combinational circuit to implement the following Boolean functions.

$$F_1 = x'y'z' + x$$

x	y	z	F
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

